

Digital Circuit Design Quiz #2

- Obtain the simplified Boolean expressions in terms of the input variables in the circuit of Fig. 1 for
 - (10%) Output F
 - (10%) Output G

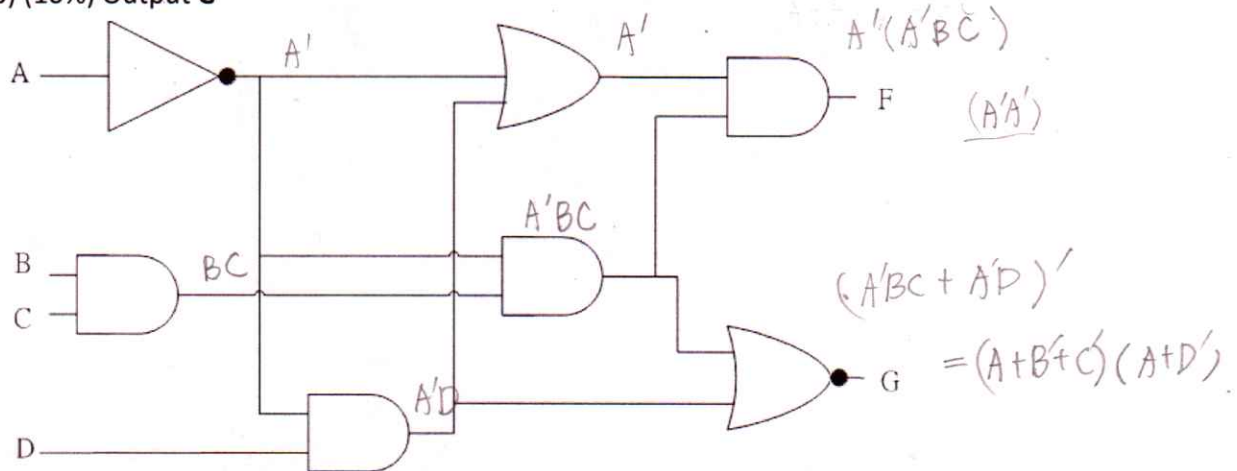


Fig.1

- (20%) Implement a full subtractor with 4×1 multiplexers.
- (20%) Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a 2-to-4-line decoder. Use block diagrams for the components.
- (20%) Implement the following Boolean function with a 8×1 multiplexer:
 - $F(A,B,C,D) = \sum(0,2,5,7,11,14)$
 - $F(A,B,C,D) = \prod(3,8,12)$
- (20%) Use an 8×1 MUX to implement a comparator that compares two 2-bit unsigned number A and B . The comparator has one output X , so that $X=1$ if $A < B$, and $X=0$ if $A \geq B$.